

materia:

fecha:

Modelo Matemático

Entrada

Salidas

$X(s)$

$Y(s)$

Oscar Nelson Loza Marca
INGENIERO EN SISTEMAS
ELECTRONICOS
R.N.I. 52.057

Oscar Nelson Loza Marca
INGENIERO EN SISTEMAS
ELECTRONICOS
R.N.I. 52.057

(2)

$X(s)$

$Y(s)$

(1)

Voltage entrada $X(s)$

$$X(s) = V_R + V_L + V_C$$

$$X(s) = R I(s) + L \frac{dI(s)}{dt} + \frac{1}{C} \int I(s) dt$$

$$\mathcal{L}\{X(s)\} = R \mathcal{L}\{I(s)\} + L \mathcal{L}\left\{\frac{dI(s)}{dt}\right\} + \frac{1}{C} \mathcal{L}\left\{\int I(s) dt\right\}$$

$$X(s) = R I(s) + L s I(s) + \frac{1}{C} \frac{I(s)}{s}$$

$$X(s) = R I(s) + L s I(s) + \frac{I(s)}{C s}$$

$$Y(s) = \frac{I(s)}{C s}$$

Transferencia

$$FT = \frac{\frac{I(s)}{C s}}{R I(s) + L s I(s) + \frac{I(s)}{C s}} \rightarrow FT = \frac{I(s) \left(\frac{1}{C s} \right)}{I(s) \left(R + L s + \frac{1}{C s} \right)}$$

$$\rightarrow FT = \frac{\frac{1}{C s}}{R + L s + \frac{1}{C s}} \rightarrow FT = \frac{1}{C s \left(R + L s + \frac{1}{C s} \right)}$$

$$\rightarrow FT = \frac{1}{C s R + L s^2 + 1}$$

Oscar Nelson Loza Marca
INGENIERO EN SISTEMAS
ELECTRONICOS
R.N.I. 52.057

(3)

materia:

fecha:

$$V_{AB} = 2V_G + 2V_L + V_C$$

$$R(0.5I_0 + 2I_0 + \frac{I_0}{2}) = \frac{1}{C} \int I_0 dt$$

$$= 2R \left(\frac{1}{2} I_0 + 2I_0 + \frac{1}{2} I_0 \right) = \frac{1}{C} I_0 t$$

$$= 2R I_0 + 2L \left(\frac{1}{2} I_0 \right) + \frac{1}{C} I_0 t$$

$$V_{AB} = 2R I_0 + 2L I_0 + \frac{I_0 t}{C}$$

$$V_{AB} = L_0 I_0$$

$$P_T = \frac{L_0 I_0^2}{2R I_0 + 2L I_0 + \frac{I_0 t}{C}}$$

$$P_T = \frac{L_0 I_0^2}{I_0 \left(2R + 2L + \frac{1}{C} \right)}$$

$$P_T = \frac{L_0}{2R + 2L + \frac{1}{C}}$$

$$P_T = \frac{L_0}{2C(1 + 2L_0 C + 1)}$$

Oscar Nelson Loza Marica
INGENIERO EN SISTEMAS
ELECTRÓNICOS
CIN. 02.057

4